

FLOATING POINT FUSED DOT PRODUCT UNIT

Guided by

Prof. Subir Roy

Submitted by

Swagatika Mahapatra (MT2018525)

Ravali Palakurthi (MT2018518)

CONTENTS:

- Introduction
- IEEE 754 format
- Floating point addition
- Floating point multiplication
- Implemented design architecture
- Kogge stone adder
- Dadda multiplier

INTRODUCTION:

- **Fused dot product:** In fused dot product unit, addition, multiplication and subtraction can be done in one hardware.

 


Fig1: Fused dot product

- **Difference between fixed and floating point numbers:**
Fixed point: Fixed number of digits after and before decimal point.
Eg: 456.88, 123.45, 456.12 etc
Floating point: Decimal point is not fixed, it varies. Wide range of numbers.
Eg: 4.5688, 45.688, 0.00045688 etc

 


Fig2: Sign, Mantissa, Exponent

 


Fig3: Fixed and floating point numbers

IEEE 754 FORMAT:

Single precision:

 


Fig4: Single precision format

- The exponent is biased by 127.(e-127)
- The normalized significand is 1.m . The binary point is before bit-22 and the one is not present explicitly.
- $S = 1 \rightarrow$ Negative number , $S = 0 \rightarrow$ Positive number
- The value of normalized number is

$$(-1)^s \times 1.m \times 2^{e-127}$$

Conversion of IEEE 754 to decimal:

Consider the following 32-bit pattern

1 1011 0110 011 0000 0000 0000 0000 0000

The value is

$$\begin{aligned} & (-1)^1 \times 2^{10110110-01111111} \times 1.011 \\ &= -1.375 \times 2^{55} \\ &= -49539595901075456.0 \\ &= -4.9539595901075456 \times 10^{16} \end{aligned}$$

FLOATING POINT ADDITION:

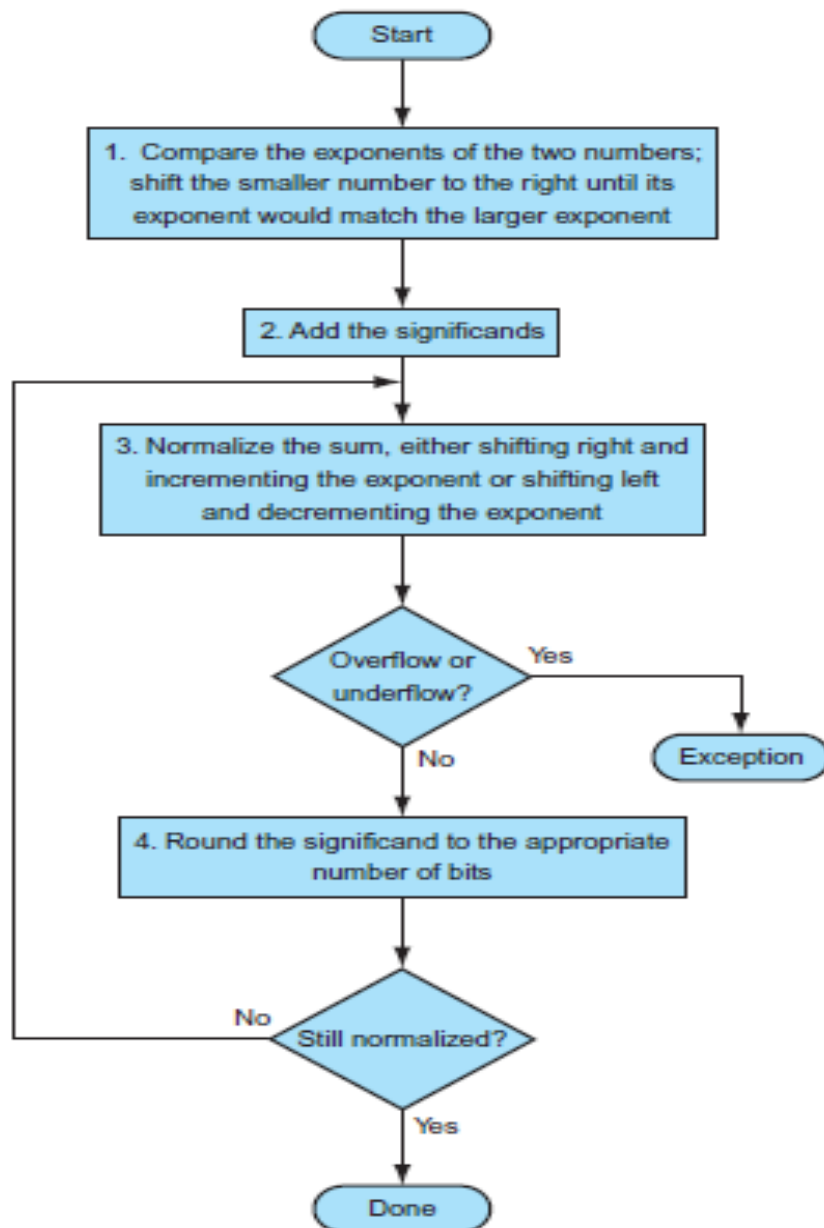


Fig5: Floating point addition

FLOATING POINT MULTIPLICATION:

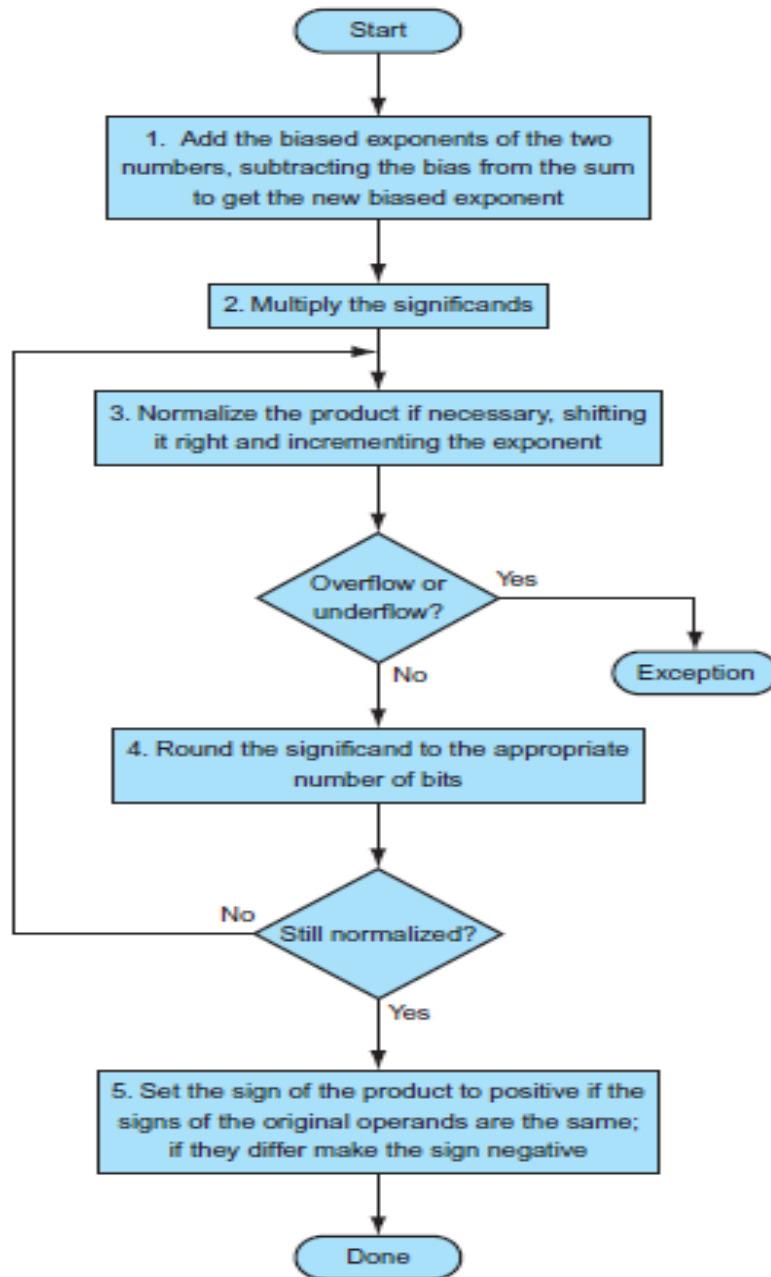


Fig6: Floating point multiplication

IMPLEMENTED DESIGN:

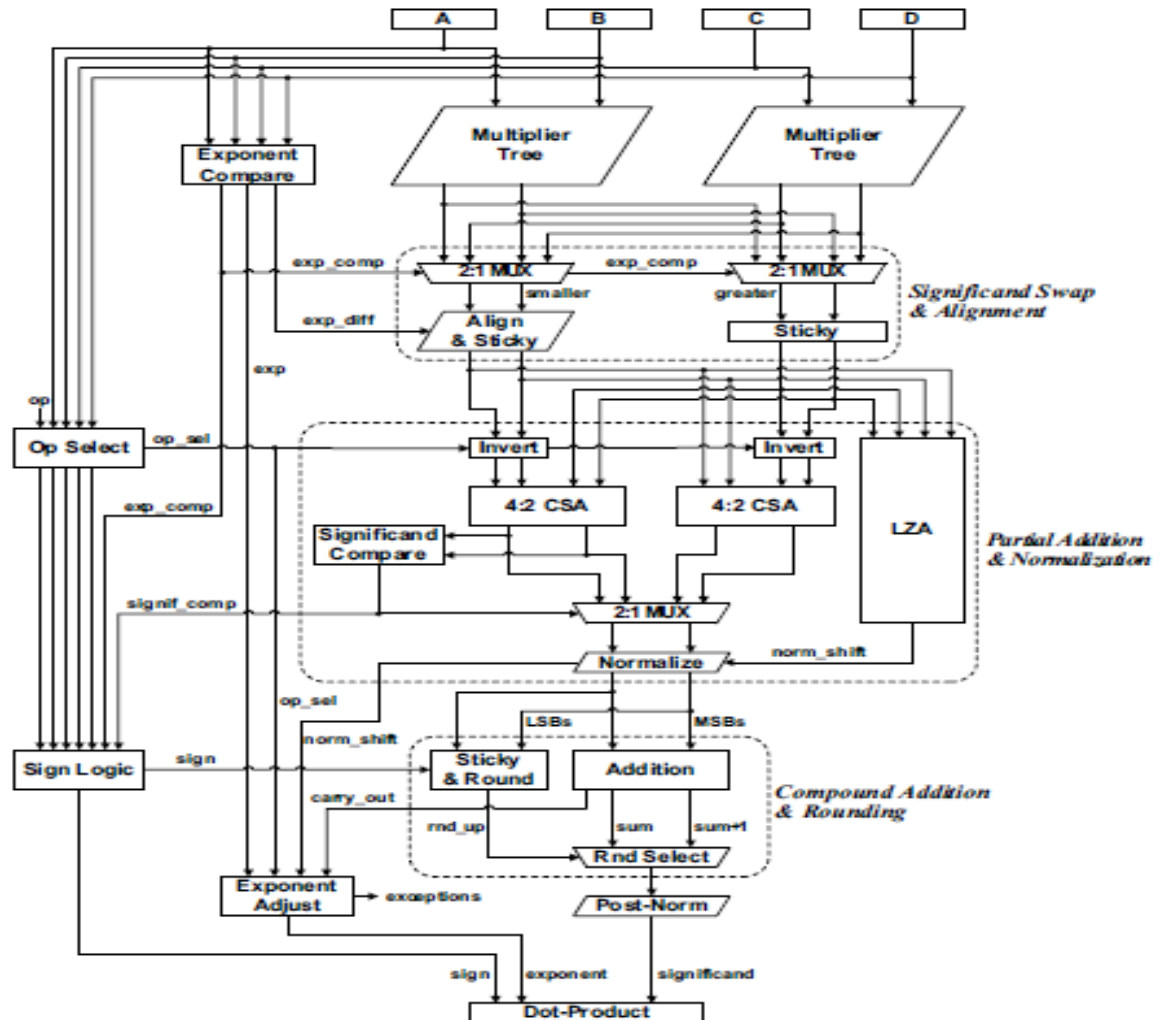


Fig7: Enhanced floating point fused dot product unit

KOGGE STONE ADDER:

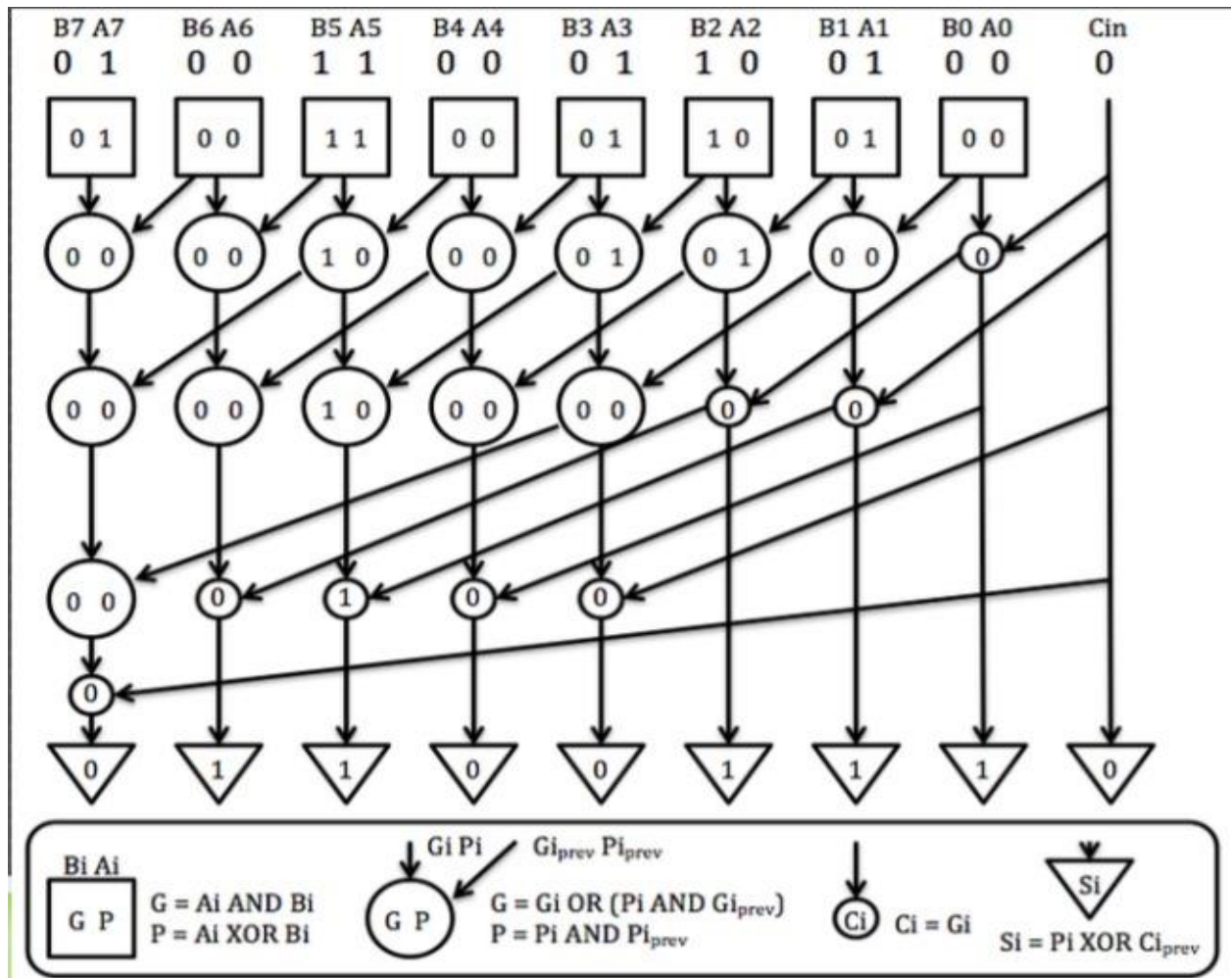


Fig8: Kogge stone adder architecture for 8 bit

Code for carry generate:

```
module grCarryGen(p1,g1,p0,g0,P,G);
input p1,g1,p0,g0;
output P,G;
wire opl;
and a1(P,p1,p0);
and a2(opl,p1,g0);
or o1(G,opl,g1);
endmodule
```


Code for carry propagate:

```
module grCarryPropagate(p1,g1,g0,G);
input p1,g1,g0;
output G;
wire opl;
and a2(opl,p1,g0);
or ol(G,opl,g1);
endmodule
```

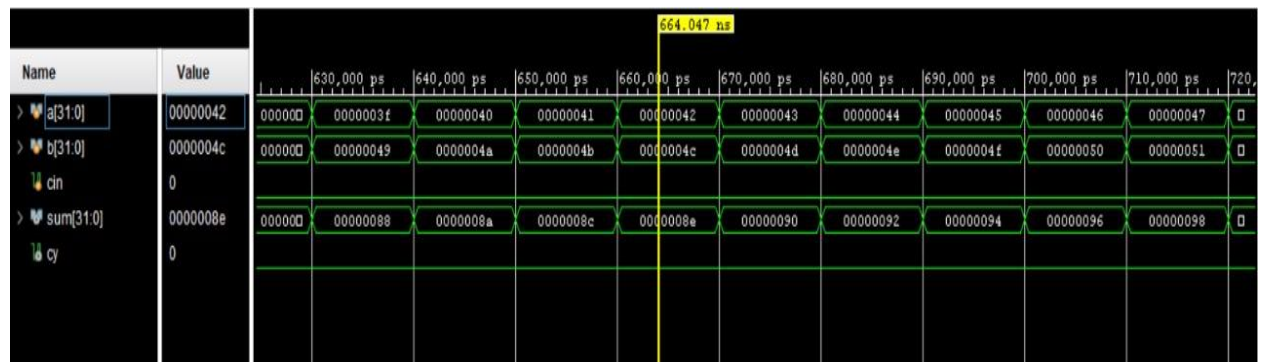


Fig9: simulation results of 32 Bit Kogge stone adder

DADDA MULTIPLIER:

- Three stages in a multiplier:
 1. Partial product generation
 2. Partial product reduction
 3. Carry propagation addition
- Dadda is a tree multiplier.
- Weight of carry is one bit higher than the weight of sum.

Bits in a multiplier (N)	Number of stages needed
3	1
4	2
5 to 6	3
7 to 9	4
10 to 13	5
14 to 19	6
20 to 28	7
29 to 42	8
43 to 63	9
64 to 94	10

Fig10:Reference table of Wallace tree multiplier

 


Fig11: Tree diagram of 8 bit Dadda multiplier

Simulation results of 24 bit Dadda multiplier

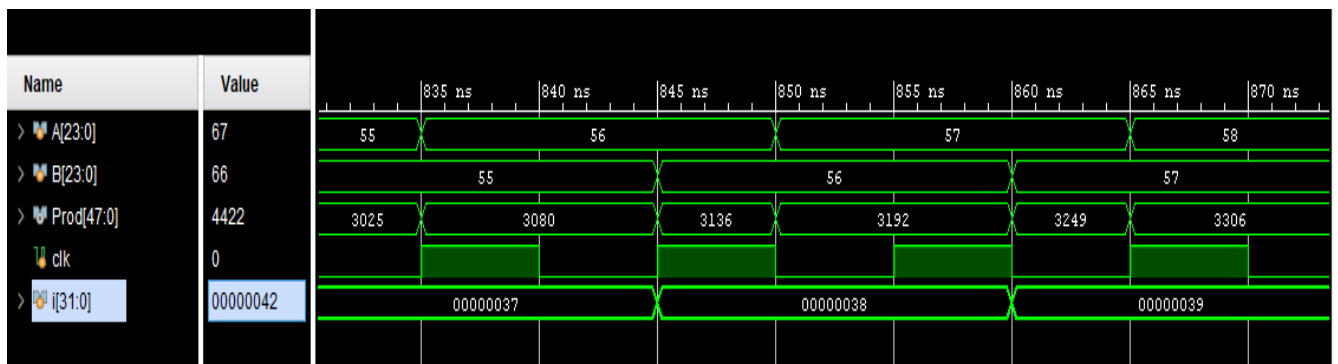


Fig12: Simulation results

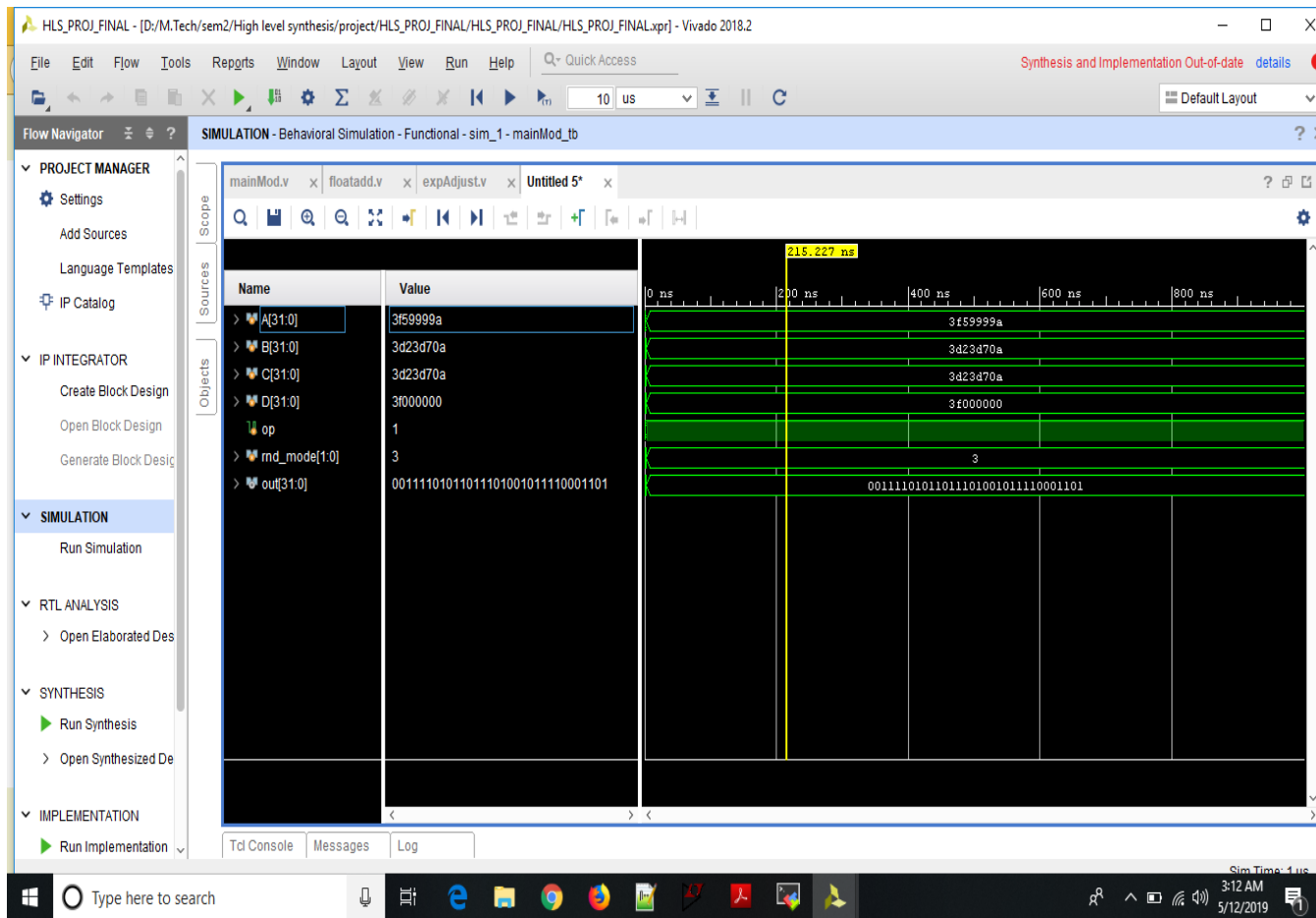


Fig.13 Simulation Result Of Fused Dot Product Unit

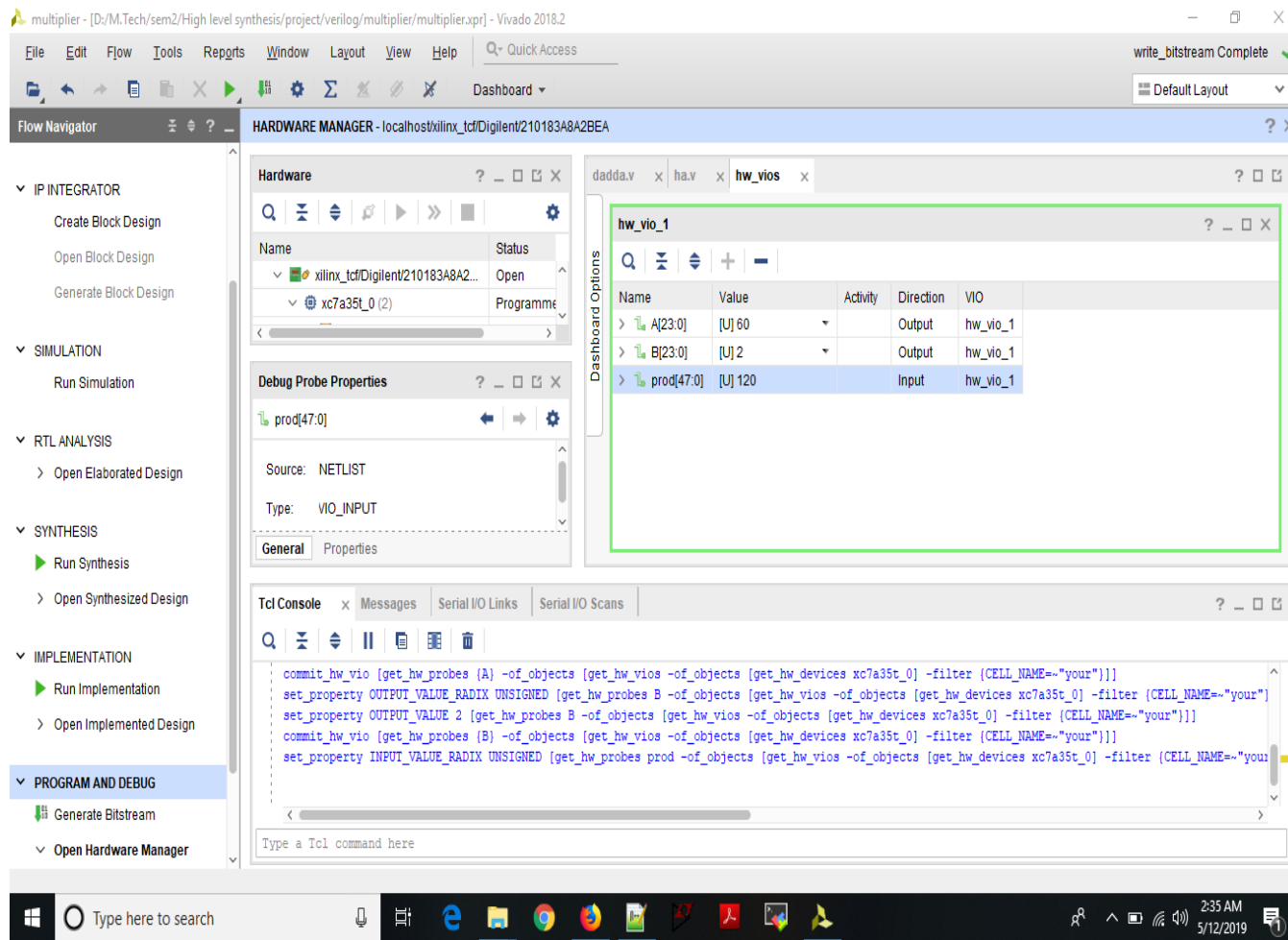


Fig.14 FPGA Implementation Of Dadda Multiplier

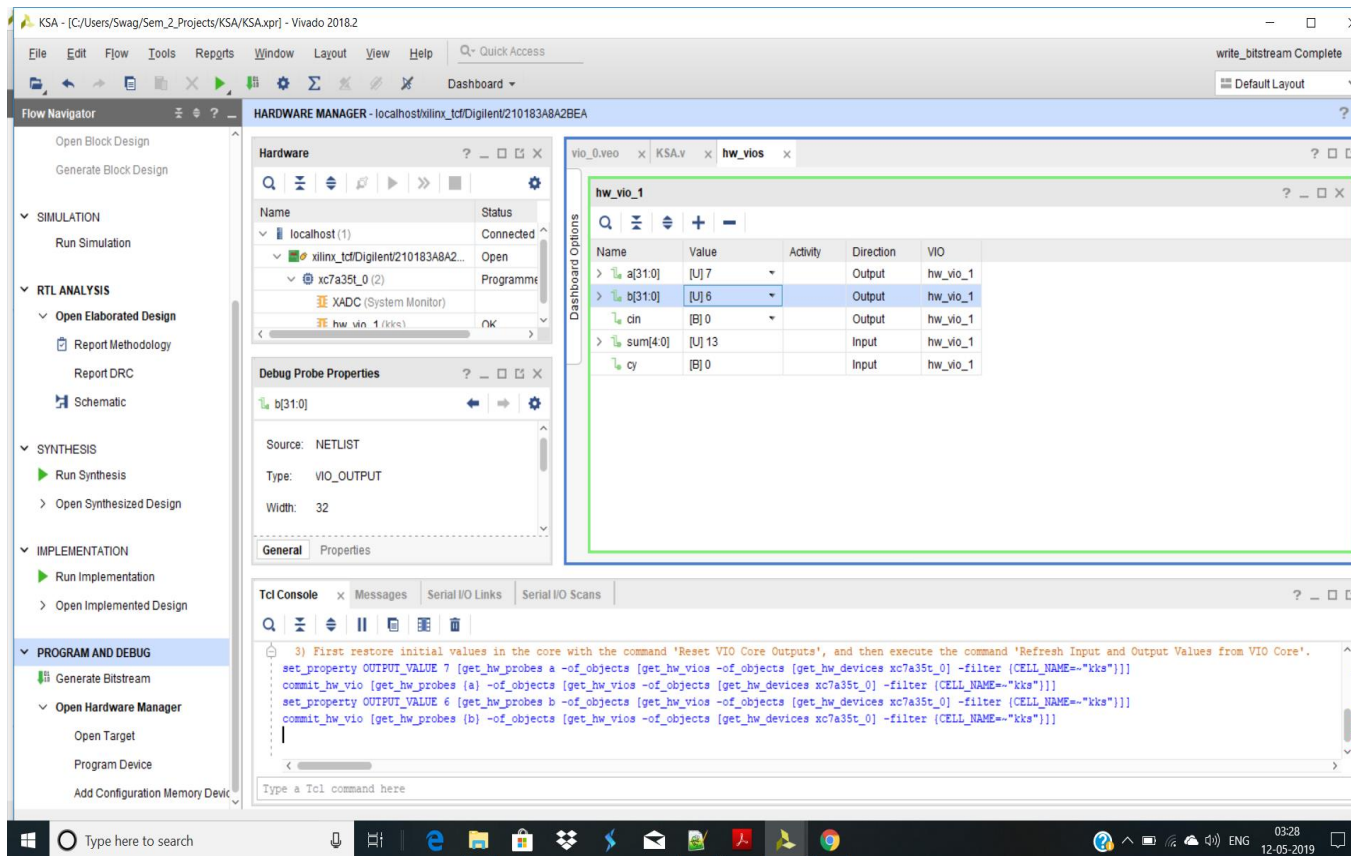


Fig.15 FPGA Implementation Of Kogge Stone Adder

Utilization Report

No of LUTs Used = 11729

On Chip Power = 0.126W

Dynamic Power = 0.117W